

1 Abstract

2 Introduction

3 Voltage dividers

We use two 10 k Ω resistors to form a resistive voltage divider. When applying a DC current, we measure $V_{in} = 6.13$ V and $V_{out} = 3.05$ V. Current is 0.30 mA. Strangely, when we apply a 1 MHz signal with $V_{pp} = 5$ V, we find extreme signal attenuation. This also occurs at 1 kHz. When we change our resistors to 1.2 k Ω , we observe a signal scaled by 1/2 as expected. We do not currently understand why 10 k Ω resistors cause such a decreased gain.

We use two 10 nF capacitors to form a capacitive voltage divider. The capacitors halve sinusoidal input signals at both 1 kHz and 1 MHz as expected. If we add a resistor to ground at the output, we expect:

$$\frac{V_{out}}{V_{in}} = \frac{1}{2 + 1/(j\omega RC)} \quad (1)$$

where j is the imaginary unit, ω is signal angular frequency (rad/s), and R and C are resistor and capacitor values (Ω , F). In effect, the circuit now behaves as a high-pass filter.

4 RC, LC, and RLC filters

Text

5 Diodes

Text

6 FM demodulator

Text